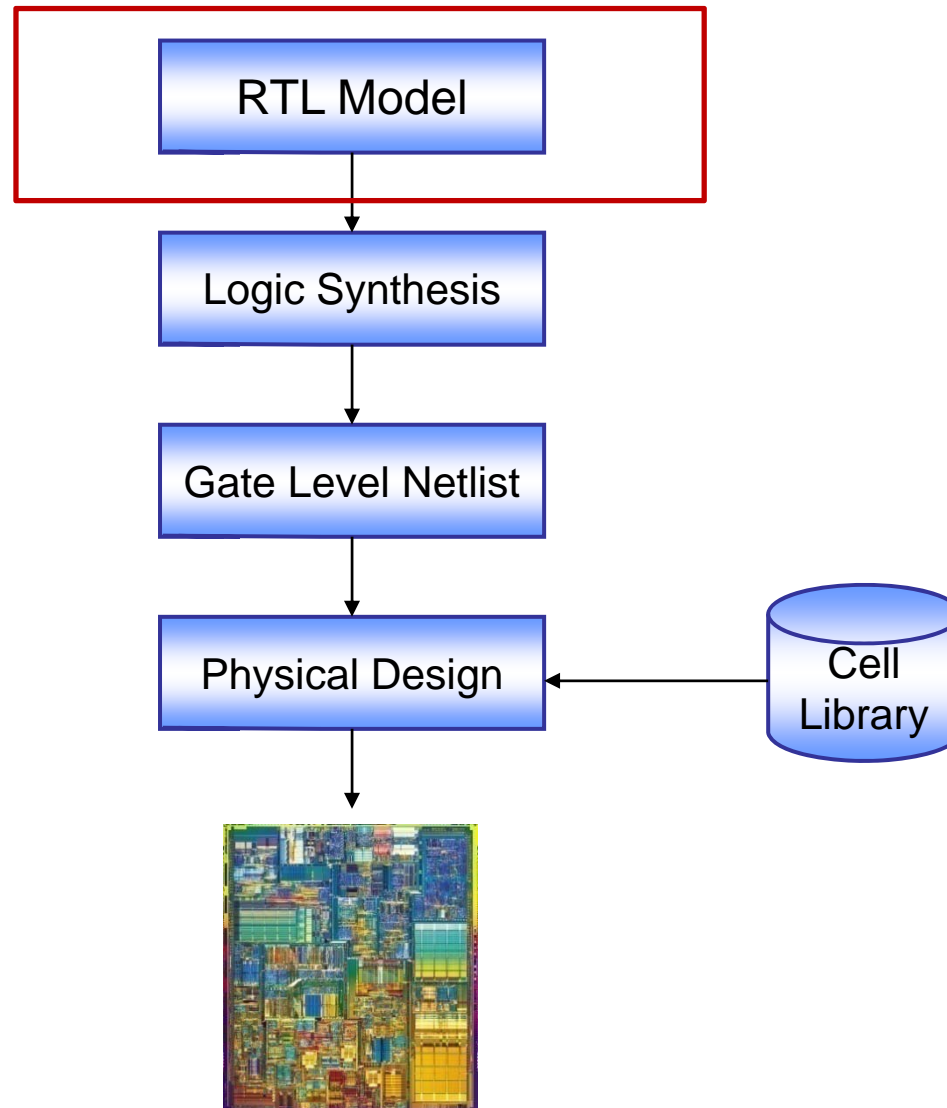


Verilog Tutorial


Outline

- Verilog & Examples
- Major Data Type
- Operations
- Behavior Modeling
- Structure Modeling

IC Design Flow



Full Adder for Example

 

```
module module_name (port_name);
```

port declaration

data type declaration



task & function declaration

module functionality or structure


timing specification

```
endmodule
```


32-bit Full Adder: example 1

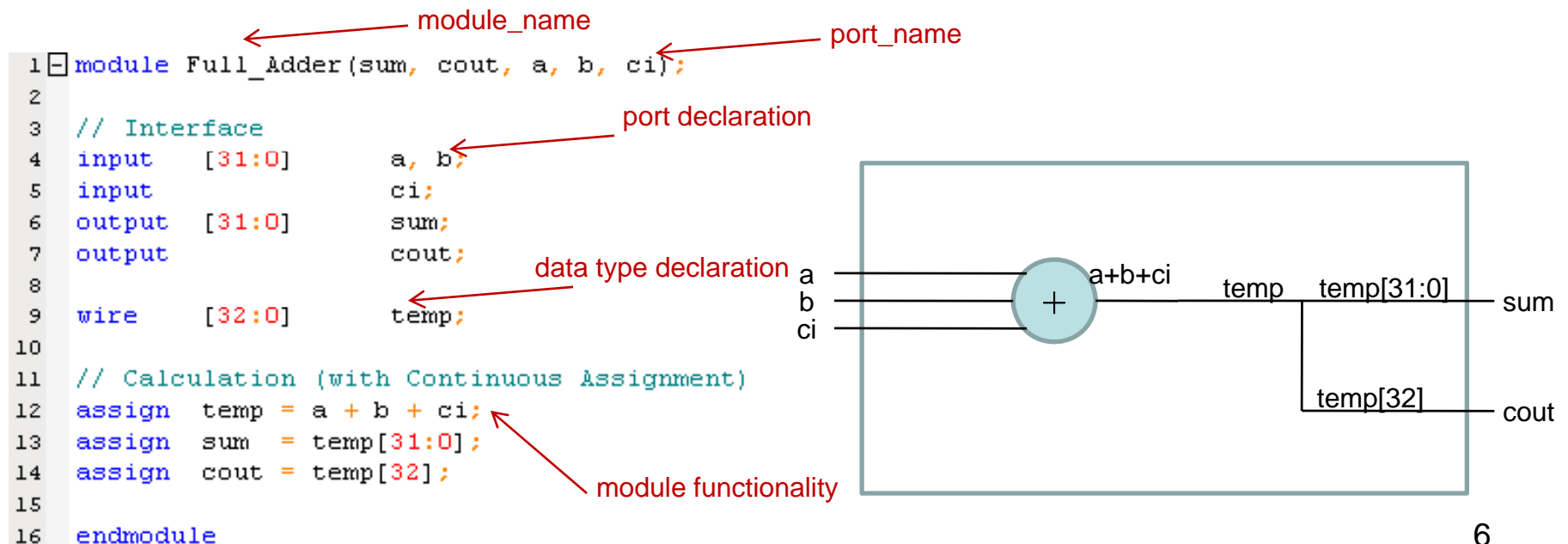 


32-bit Full Adder: example 2

 

 
```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 output [31:0]    sum;
7 output          cout;
8
9 // Calculation (with Continuous Assignment)
10 assign {cout, sum} = a + b + ci;
11
12 endmodule
```



32-bit Full Adder: example 3

 
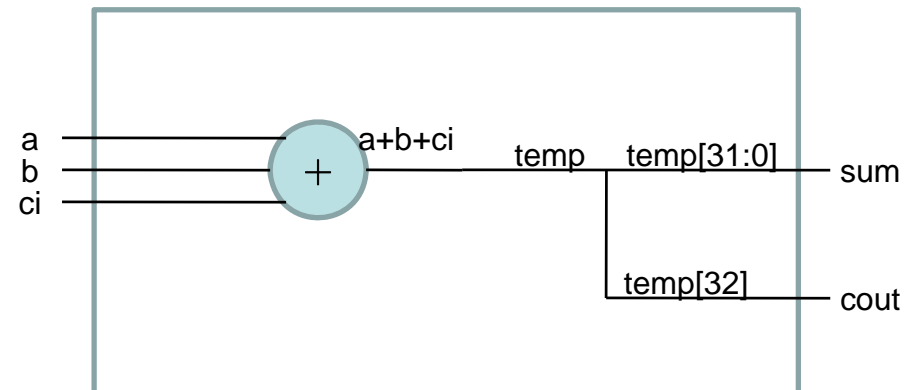
```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 output [31:0]    sum;
7 output          cout;
8
9 reg  [32:0]      temp;
10
11 assign sum = temp[31:0];
12 assign cout = temp[32];
13
14 // Calculation (with Always Procedural Block)
15 always@(a or b or ci) begin
16     temp = a + b + ci;
17 end
18
19 endmodule
```



Wire & Register

- Can not use “reg” in left-hand side of continuous assignment.
- Can not use “wire” in left-hand side of assignment in procedural block.


```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 output [31:0]    sum;
7 output          cout;
8
9 reg  [32:0]      temp;
10
11 // Calculation (with Continuous Assignment)
12 assign temp = a + b + ci;
13 assign sum  = temp[31:0];
14 assign cout = temp[32];
15
16 endmodule
```

** Error: (12): Register is illegal in left-hand side of continuous assignment


```
1 module Full_Adder(sum, cout, a, b, ci);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 output [31:0]    sum;
7 output          cout;
8
9 wire [32:0]      temp;
10
11 assign sum  = temp[31:0];
12 assign cout = temp[32];
13
14 // Calculation (with Always Procedural Block)
15 always@(a or b or ci) begin
16     temp = a + b + ci;
17 end
18
19 endmodule
```

** Error: (13): (vlog-2110) Illegal reference to net "temp"

64-bit Full Adder

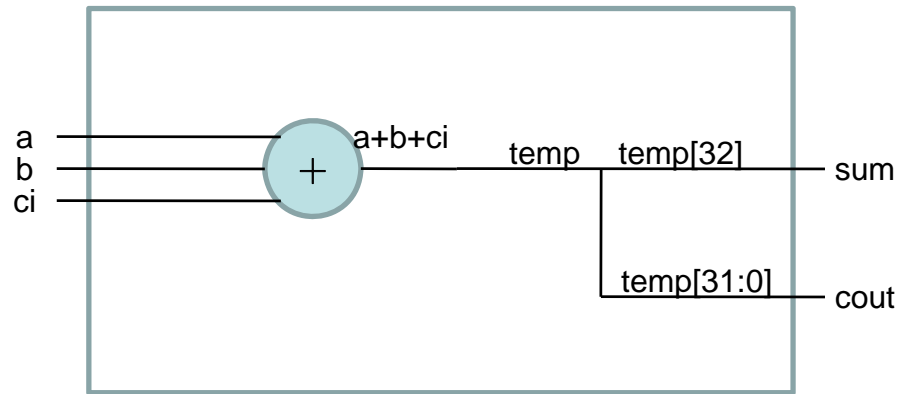

Full_Adder

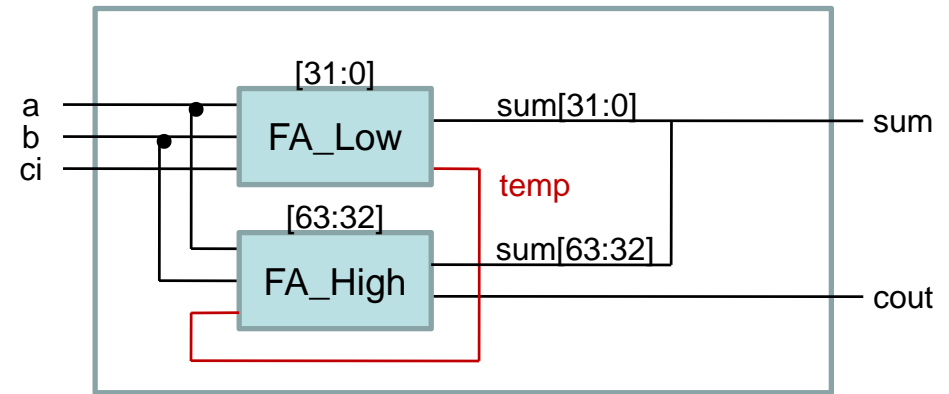

Full_Adder_64

```

1 module Full_Adder(sum, cout, a, b, ci);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 output [31:0]    sum;
7 output          cout;
8
9 reg  [32:0]      temp;
10
11 assign sum = temp[31:0];
12 assign cout = temp[32];
13
14 // Calculation (with Always Procedural Block)
15 always@(a or b or ci) begin
16     temp = a + b + ci;
17 end
18
19 endmodule

```


```

1 module Full_Adder_64(sum, cout, a, b, ci);
2
3 // Interface
4 input  [63:0]    a, b;
5 input          ci;
6 output [63:0]    sum;
7 output          cout;
8
9 wire          temp;
10
11 // Calculation (with 32-bit Full Adder Module)
12 Full_Adder FA_Low (sum[31:0], temp, a[31:0], b[31:0], ci);
13 Full_Adder FA_High(sum[63:32], cout, a[63:32], b[63:32], temp);
14
15 endmodule

```


Test Your 64-bit Full Adder Module

Testbench

 


```

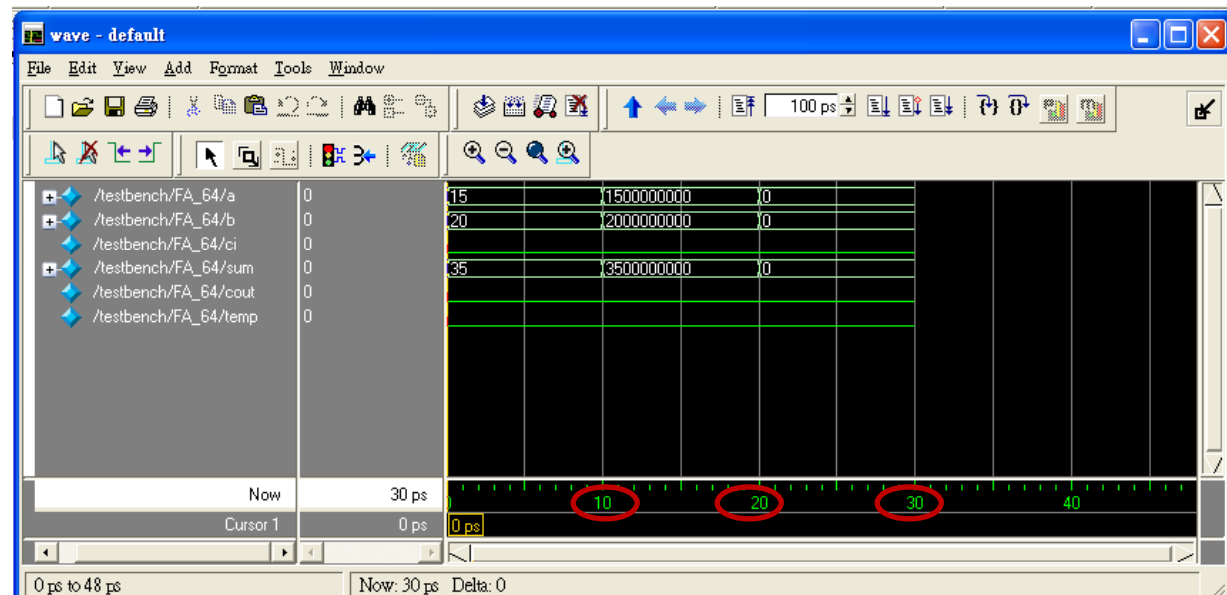1 module testbench();
2
3 reg [63:0] a, b;
4 reg
5 wire [63:0] sum;
6 wire
7
8 initial begin
9     a = 15;
10    b = 20;
11    ci = 0;
12    #10 ← Delay period
13    a = 1500000000;
14    b = 2000000000;
15    ci = 0;
16    #10
17    a = 0;
18    b = 0;
19    ci = 0;
20    #10
21    $stop();
22 end
23
24 // Add your modules here:
25 Full_Adder_64 FA_64(sum, cout, a, b, ci);
26
27 endmodule
  
```




32-bit Adder Subtractor: example 1

 


```

1 module Adder_Subtractor(sum, cout, a, b, ci, sel);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 input          sel;
7 output [31:0]    sum;
8 output          cout;
9
10 reg  [32:0]      temp;
11
12 assign sum = temp[31:0];
13 assign cout = temp[32];
14
15 // Calculation (with Always Procedural Block)
16 always@(a or b or ci or sel) begin
17     if(sel) begin
18         temp = a - b - ci;
19     end
20     else begin
21         temp = a + b + ci;
22     end
23 end
24
25 endmodule


```

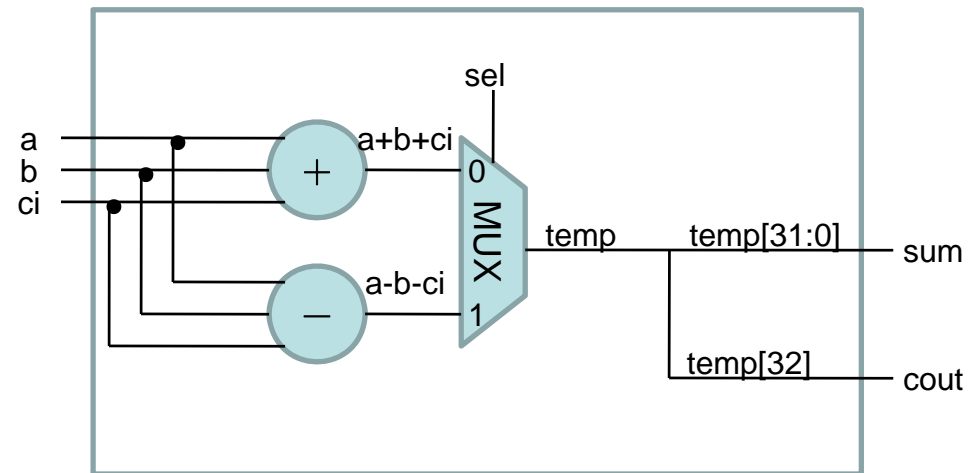

32-bit Adder Subtractor: example 2

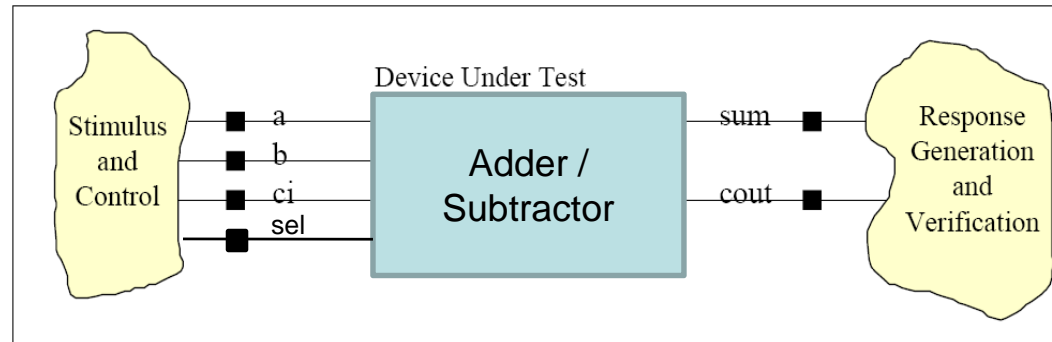

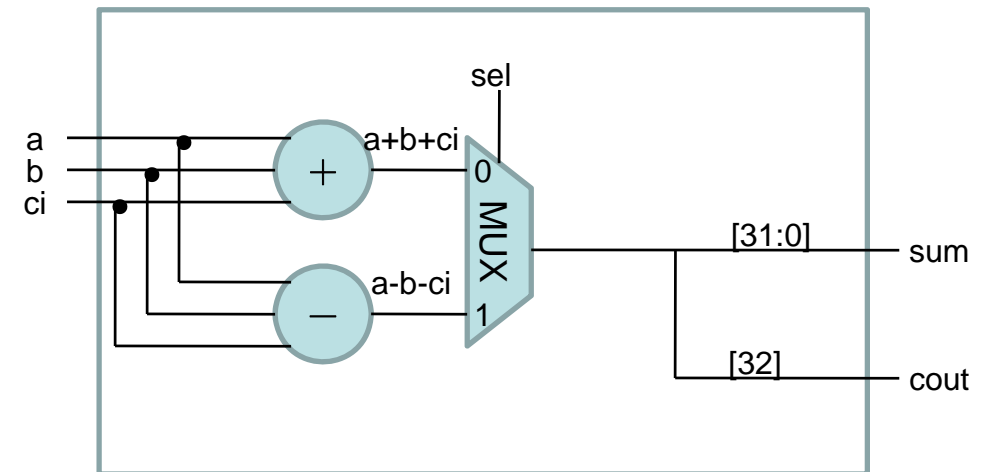
```
1 module Adder_Subtractor(sum, cout, a, b, ci, sel);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 input          sel;
7 output [31:0]    sum;
8 output          cout;
9
10 // Calculation (with Continuous Assignment)
11 assign {cout, sum} = (sel) ? a-b-ci : a+b+ci;
12
13 endmodule
```



Test Your 64-bit Adder Subtractor Module


Testbench

 


```

1 module testbench();
2
3   reg   [63:0]    a, b;
4   reg           ci;
5   reg           sel;
6   wire  [63:0]    sum;
7   wire          cout;
8
9   initial begin
10      a = 15;
11      b = 20;
12      ci = 0;
13      sel = 0;
14      #10
15      a = 1500000000;
16      b = 2000000000;
17      ci = 0;
18      sel = 1;
19      #10
20      a = 0;
21      b = 0;
22      ci = 0;
23      sel = 0;
24      #10
25      $stop();
26   end
27
28   // Add your modules here:
29   Adder_Subtractor_64 AS_64(sum , cout, a, b, ci, sel);
30
31 endmodule

```

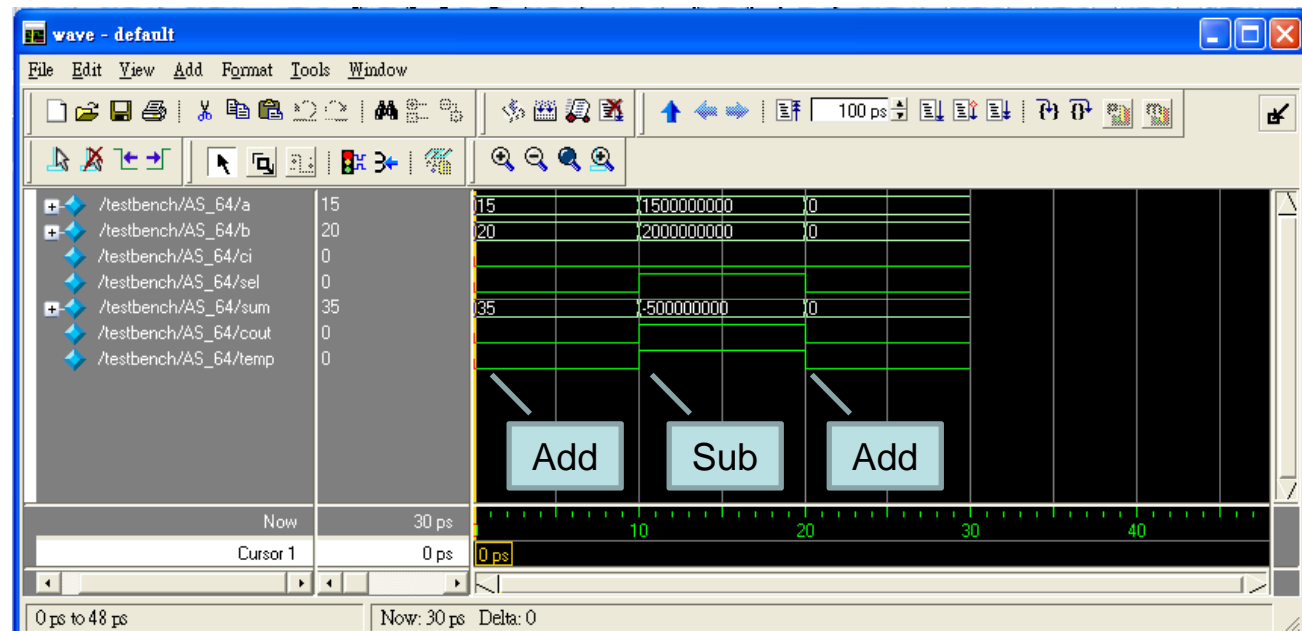

32-bit Adder Subtractor with Clock

 


```

1 module Adder_Subtractor(sum, cout, a, b, ci, sel, clk);
2
3 // Interface
4 input  [31:0]    a, b;
5 input          ci;
6 input          sel;
7 input          clk;
8 output [31:0]    sum;
9 output          cout;
10
11 reg  [32:0]      temp;
12
13 assign sum = temp[31:0];
14 assign cout = temp[32];
15
16 // Calculation (with Always Procedural Block)
17 always@(posedge clk) begin
18     if(sel) begin
19         temp <= a - b - ci;
20     end
21     else begin
22         temp <= a + b + ci;
23     end
24 end
25
26 endmodule


```

Use non-blocking assignment !

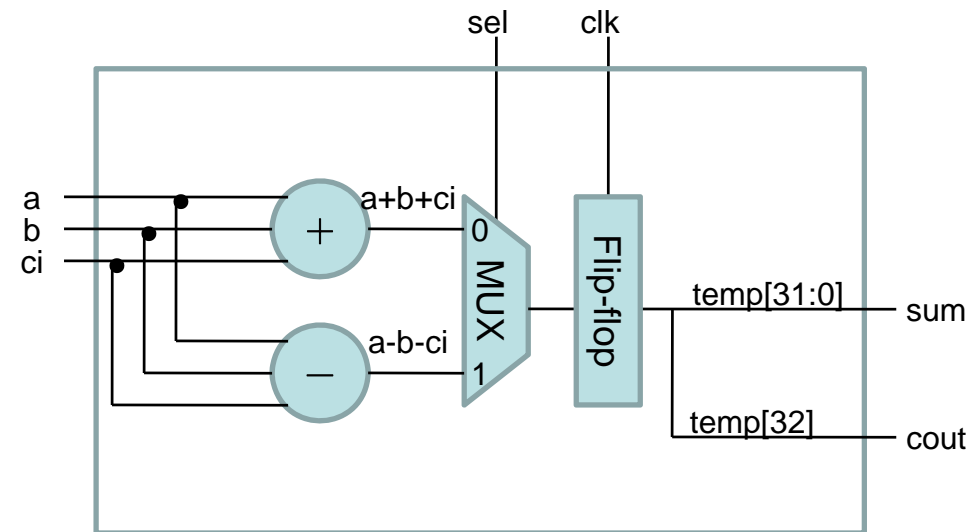

Test 32-bit Adder Subtractor with Clock

```
1 module testbench();
2
3   reg    [31:0]    a, b;
4   reg          ci;
5   reg          sel;
6   reg          clk;
7   wire  [31:0]    sum;
8   wire          cout;
9
10  always #5 clk = ~clk;
11
12  initial begin
13    clk = 0;
14    #1
15    a = 15;
16    b = 20;
17    ci = 0;
18    sel = 0;
19    #10
20    a = 15000;
21    b = 20000;
22    ci = 0;
23    sel = 1;
24    #10
25    a = 0;
26    b = 0;
27    ci = 0;
28    sel = 0;
29    #10
30    $stop();
31  end
32
33  // Add your modules here:
34  Adder_Subtractor AS(sum, cout, a, b, ci, sel, clk);
35
36 endmodule
```

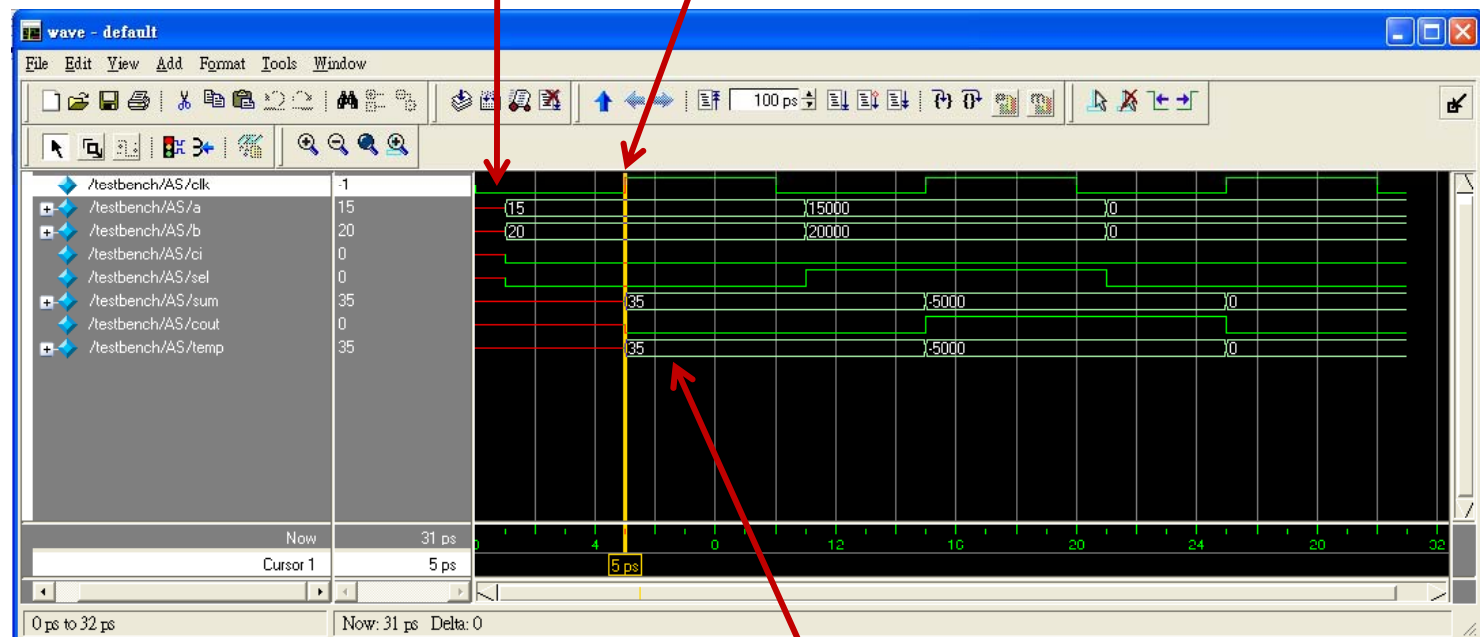

Outline


- Verilog & Examples
- Major Data Type
- Operations
- Behavior Modeling
- Structure Modeling

Major Data Type

- Nets (Wires)
- Registers
- Parameters


Nets

 - *Net* data type represent physical connections between structural entities.
- A *net* must be driven by a driver, such as a gate or a **continuous assignment**.
- Verilog automatically propagates new values onto a net when the drivers change value.



Registers

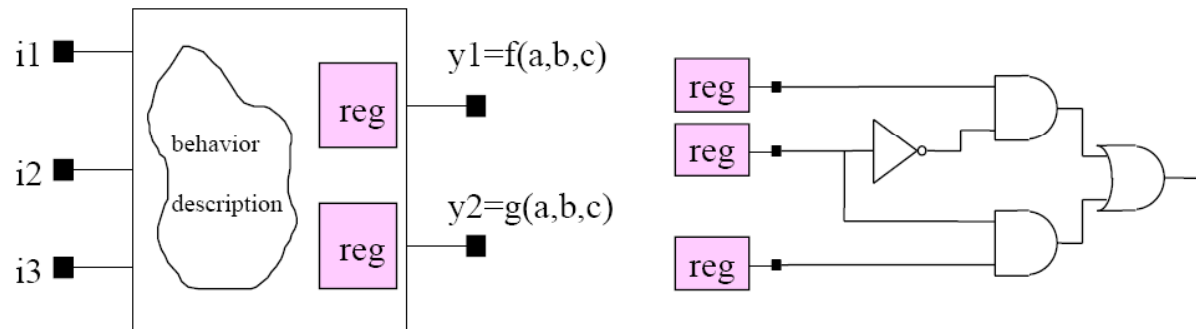- Registers represent abstract storage elements.
- A register holds its value until a new value is assigned to it.
- Registers are used extensively in **behavior modeling**.




Common Mistake in Choosing Data Type

- An output port can be driven by a net or a register, but it can only drive a net.

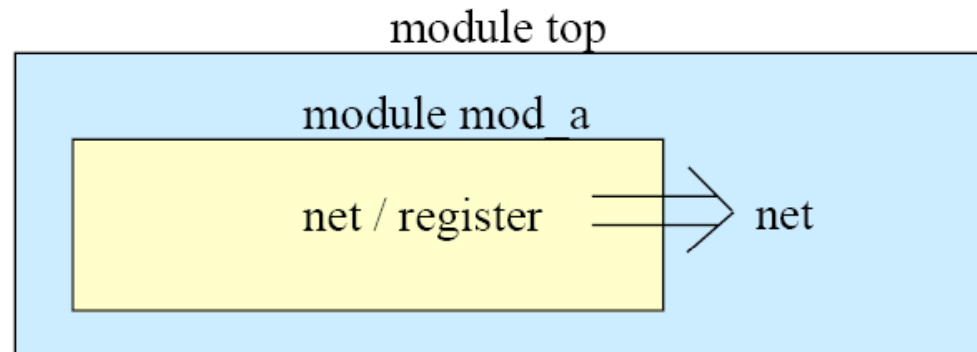Example

```
module top (...);  
....  
reg rega, regb;  
  
mod_a U1(rega, regb);  
.....
```




instance *U1*'s output port
connect to a register *rega*.

Parameters

- Parameters are not variables, they are constants.
- Typically parameters are used to specify delays and width of variables.

```
module var_mux(out, i0, i1, sel) ;  
  parameter width = 2, delay = 1 ;  
  output [width-1:0] out ;  
  input  [width-1:0] i0, i1 ;  
  input  sel;  
  
  assign #delay out = sel ? i1 : i0 ;  
endmodule
```

- 
- if *sel* = 1, then *i1* will be assigned to *out*;
 - if *sel* = 0, then *i0* will be assigned to *out*;

Integer & Real Numbers

16 --- 32 bits decimal

8'd16

8'h10

8'b0001_0000

8'o20

32'bx --- 32 bits x

2'b1? --- “?” represents a high impedance bit

6.3

5.3e-4


6.2E3

Outline

- Verilog & Examples
- Major Data Type
- **Operations**
- Behavior Modeling
- Structure Modeling

Continuous Assignments

 - Any changes in the RHS of the continuous assignment are evaluated and the LHS is updated.



Example

- RHS can be
 - Expression
 - assign and_out = i1 & i2;
 - Value
 - assign net_1 = 1;
 - Other net
 - assign net_a = net_b;

continuous assignment

```
module inv_array(out, in);
    output [31:0] out;
    input  [31:0] in;

    assign out = ~in;
endmodule
```

gate-level modeling

```
module inv_array(out, in);
    output [31:0] out;
    input  [31:0] in;

    not G0(out[0], in[0]);
    .....
    not G31(out[31], in[31]);
endmodule
```


Operations

arithmetic operator

operator	operation
+	arithmetic addition
-	arithmetic subtraction
*	arithmetic multiplication
/	arithmetic division
%	arithmetic modulus

other operators

operator	operation
>>	logical shift right
<<	logical shift left
==, !=	equality
===, !==	identity
?:	conditional
{}	concatenate
{{}}	replicate

unary operator (1-bit result)

operator	operation
&	unary reduction AND
~&	unary reduction NAND
	unary reduction OR
~	unary reduction NOR
^	unary reduction XOR
~^	unary reduction XNOR

- unary operation will perform the operation on each bit of the operand and get a one-bit result.

|8'b00101101 is 1'b1

bit-wise operators

operator	operation
~	bit-wise NOT
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~^	bit-wise XNOR

- binary bit-wise operation will perform the operation one bit of a operand and its equivalent bit on the other operand to calculate one bit for the result.

(8'b11110000 & 8'b00101101) is 8'b00100000

logical operators

operator	operation
!	logical NOT
&&	logical AND
	logical OR
==	logical equality
!=	logical inequality
===	logical identity
!==	the inverse of ===

- logical operator operate with logic values. (non-zero is true, and zero value is false).

if(sel == 4'h03) else

Shift Operator


```
module shift_register(reg_out, reg_in);  
    output [5:0] reg_out;  
    input  [5:0] reg_in;  
  
    parameter shift = 3;  
    assign reg_out = reg_in << shift;  
endmodule
```

examples :

```
reg_in = 6'b011100  
reg_in << 3 → 100000  
reg_in >> 3 → 000011
```

Conditional Operator
 
```
module MUX4_1(out, i0, i1, i2, i3, sel);  
    output [3:0] out;  
    input  [3:0] i0, i1, i2, i3;  
    input  [1:0] sel;  
  
    assign out = (sel == 2'b00) ? i0 :  
                 (sel == 2'b01) ? i1 :  
                 (sel == 2'b10) ? i2 :  
                 (sel == 2'b11) ? i3 :  
                 4'bx;  
endmodule
```



Concatenation & Replication Operator

▼ Concatenation operator in LHS

```
module add_32 (co, sum, a, b, ci);  
    output co;  
    output [31:0] sum;  
    input  [31:0] a, b;  
    input  ci;  
    assign #100 {co, sum} = a + b + ci;  
endmodule
```

▼ Bit replication to produce *01010101*

```
assign byte = {4{2'b01}};
```

▼ Sign Extension

```
assign word = {{8{byte[7]}} , byte};
```

Outline

- Verilog & Examples
- Major Data Type
- Operations
- Behavior Modeling
- Structure Modeling

Behavior Modeling

- At system level, system's **functional view** is more important than implementation.
 - You do not have any idea about how to implement your netlist.
 - The data flow of this system is analyzed,
 - You may need to explore different design options.
- Behavior modeling enables you to describe the system at a **high-level of abstraction**.
- All you need to do is to describe the behavior of your design.


Behavior Modeling

- In behavior modeling, you must describe your circuits'...
 - Action
 - How do you model your circuit's behaviors?
 - Timing control
 - At what time do what thing.
 - At what condition do what thing.
- Verilog supports the following constructs to model circuits' behavior
 - Procedural block
 - Procedural assignment
 - Timing control
 - Control statement

Procedural Blocks

- In Verilog, procedural blocks are the basic of behavior modeling.
 - You can describe one behavior in one procedural block
- Procedural blocks are of two types
 - Initial procedural block
 - Which execute only once
 - Always procedural block
 - Which execute in a loop


initial		c
c	_____	
c	_____	
c	_____	
c	_____	

 

always		c
c	_____	
c	_____	
c	_____	
c	_____	

Procedural Blocks (Cont.)

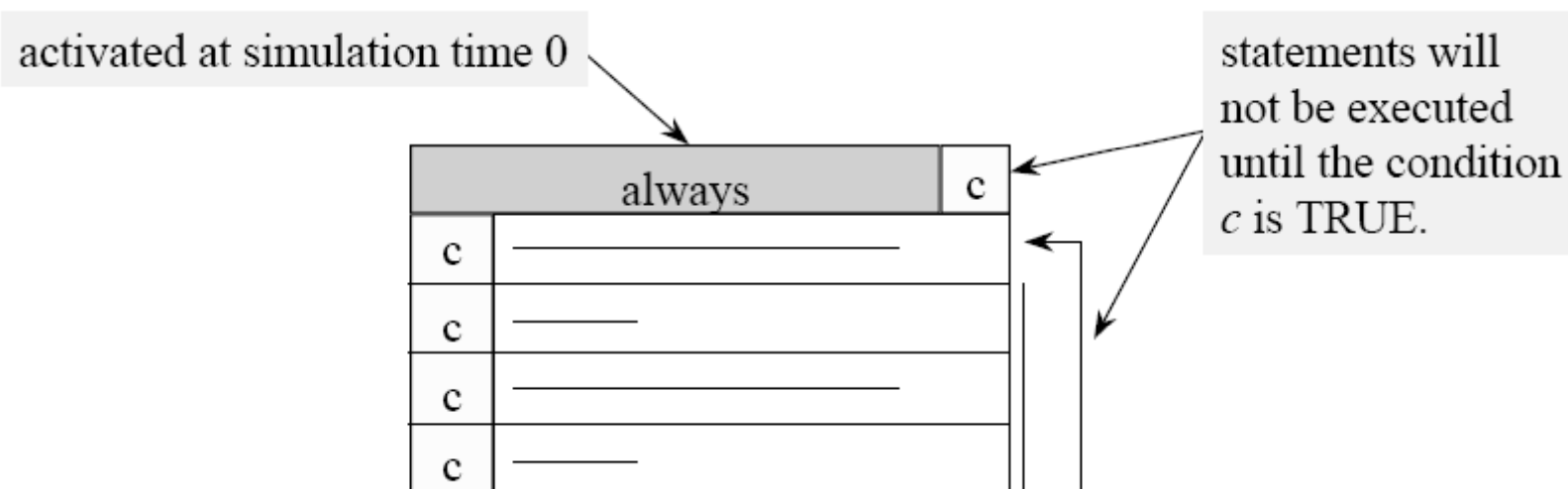- All procedural blocks are activated at simulation time 0
 - With enabling condition, the block will not be executed until the enabling condition evaluates to TRUE
 - Without enabling condition, the block will be executed immediately.




Procedural Blocks (Cont.)

```
module clock_gen (phi1, phi2);  
  output phi1, phi2;  
  reg phi1, phi2;
```

```
  initial begin  
    phi1 = 0; phi2 = 0;  
  end
```

```
  always #100 phi1 = ~ phi1;
```
 
```
  always @(posedge phi1)  
  begin  
    phi2 = 1;  
    #50 phi2 = 0;  
    #50 phi2 = 1;  
    #50 phi2 = 0;  
  end  
endmodule
```



These procedural blocks are activated and executed at simulation time 0.

This procedural block is activated at simulation time 0 but executed at positive edge of *phi1*.


Procedural Assignment

- Procedural assignments drive values or expressions onto registers.

```
module adder32 (sum, carry, a, b, ci);  
    output [31:0] sum;  
    output carry;  
    input [31:0] a, b;  
    input ci;  
    reg [31:0] sum;  
    reg carry;
```

```
    always @ (a or b or ci)  
        { carry, sum } = a + b + ci;  
endmodule
```

procedural assignment




Procedural Assignments


- A continuous assignment statement **cannont** be inside procedural blocks.
- A procedural assignment statement **must** be inside procedural blocks.

```
module f_adder (sum, co, a, b, ci);  
    output sum, co;  
    input  a, b, ci;  
    reg sum;  
  
    sum = a ^ b ^ ci;  
    always @(a or b or ci)  
        assign co = (a & b) | (b & ci) | (ci & a);  
endmodule
```

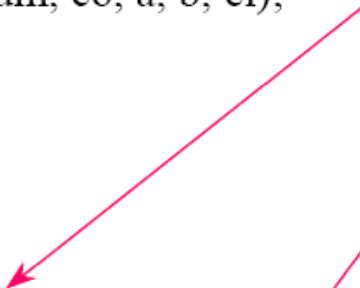Error! Illegal left-hand-side continuous assignment.



Error! Illegal left-hand-side in assign statement



Non-blocking Procedural Assignment

- Blocking procedural assignment

```
always@(posedge clock) begin
    x = a;
    y = x;
    z = y;
end
```

$x = a$ $x = a$
 $y = x \rightarrow y = x$
 $z = y$ $z = x$

- Non-blocking procedural assignment

```
always@(posedge clock) begin
    x <= a;
    y <= x;
    z <= y;
end
```

Shift register
 $x = a$
 $y = x_{old}$
 $z = y_{old}$

Conditional Statements

- If and If-Else Statement

Example

```
if (expression)
    statement
else
    statement
```

```
if (rega >= regb)
    result = 1;
else
    result = 0;
```

```
if (expression)
    statement
else if (expression)
    statement
else
    statement
```

```
if (index > 0)
    if (rega > regb)
        result = rega;
    else
        result = 0;
else
    $display("* Warning * index is equal or small than 0!");
```

Conditional Statements

- Case Statement

```
`define pass_accum 4'b0000  
`define pass_data 4'b0001  
`define ADD 4'b0010
```

```
case (opcode)  
  `pass_accum : #3.5 alu_out = accum;  
  `pass_data  : #3.5 alu_out = data;  
  `ADD        : #3.5 alu_out = accum + data;  
  `AND        : #3.5 alu_out = accum & data;  
  `XOR        : #3.5 alu_out = accum ^ data;  
  default     : #3.5 alu_out = 8'bx;  
endcase
```


Outline

- Verilog & Examples
- Major Data Type
- Operations
- Behavior Modeling
- Structure Modeling


Structure Modeling

- In structural modeling, you connect components with each other to create a more complex component.

half adder

 


full adder

 

Structure Modeling


half adder

 

```
module HA(a,b,sum,co);  
  input a, b;  
  output sum, co;  
  assign sum = a ^ b;  
  assign co = a & b;  
endmodule
```

HA.v

full adder

 

```
module FA(A,B,CarryIn,Sum,CarryOut);  
  input A, B, CarryIn;  
  output Sum, CarryOut;  
  wire sum0, sum1, co0;  
  HA ha0(A,B,sum0,co0);  
  HA ha1(co0,CarryIn,sum1,CarryOut);  
  assign Sum = sum0 ^ sum1;  
endmodule
```

43
FA.v